

# Synthesis of control circuits from STG specifications

## Practical Exercise Manual

J. Cortadella   M. Kishinevsky   A. Kondratyev   L. Lavagno  
 A. Yakovlev

ASYNC 2003, Vancouver

### 1 Task 1: Handshake communication

#### 1.1 What is Half-handshake?

Figure 1 shows a data processing structure consisting of two computation blocks,  $A$  and  $B$ , and a control circuit. Signals  $Ri$  and  $Ai$  are inputs, and  $Ao$  and  $Ro$  are outputs of the control. Output  $Ro$  can be seen as a latch enable signal for the data path. Output  $Ao$  is an acknowledgement signal sent to the previous control stage. The goal is to design the speed-independent control circuit. A number of different control disciplines are possible. Let us choose a discipline based on handshaking between adjacent stages, for instance the one described by the Timing Diagram shown in Figure 2. Let us call it *half-handshake*. This discipline assumes the following:

1. The datapath includes latches which are *transparent* to input data when the control signal is low and which are *opaque*, i.e. insensitive to its data input, when the control is high. E.g., the latch in  $B$  is transparent when  $Ro = 0$  and opaque when  $Ro = 1$ .
2. The fact that  $Ri$  becomes 1 indicates that the data in the previous stage, stage  $A$ , is captured and stable (after the previous stage has become opaque).

Additional assumptions could be made if needed, depending on our knowledge of the implementation of the latches and delays in the datapath. For example, we may need to assume that there is sufficient delay between the appearance of data on the data bus between stages and the rising edge on  $Ri$ , and hence on  $Ro$ , in order to guarantee the appropriate setup conditions for the latch in stage  $B$ .

The STG specifying the half-handshake control circuit is given in Figure 3. Signals  $Ri$  and  $Ai$  are inputs, and  $Ao$  and  $Ro$  are outputs. Output  $Ro$  can be seen as a latch enable signal for the data path. Output  $Ao$  is an acknowledgement signal sent to the previous control stage.

 


Figure 1: A data processing structure.

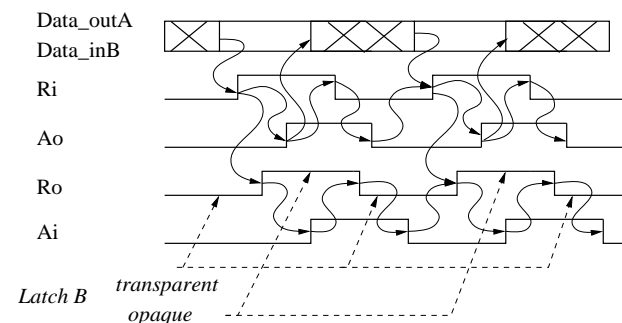


Figure 2: Half-handshake discipline: timing diagram.

 


Figure 3: An STG for the half-handshake: (a) independent handshakes at the left and right ports (b) unbounded version with  $Ri+ \rightarrow Ro+$ , (c) version with CSC-violation, (d) final version with CSC and a redundant arc removed

## 1.2 Exercise

1. Construct an STG specification (in `astg` format) for half-handshake control following steps presented in Figure 3. Save this specification in file `half-hand.g`. (Alternatively, find a sample solution `half-hand.g` in directory `solutions` and examine it carefully. Note the lines which will need to be commented out to illustrate various effects, such as unboundedness and CSC-violations.)
2. Display your STG using the `draw_astg` tool. For that, use the following commands and compare their effects:

```
draw_astg half-hand.g | ghostview -
draw_astg -nofold half-hand.g | ghostview -
draw_astg -noinfo -bw half-hand.g | ghostview -
draw_astg half-hand.g -o half-hand.g.ps
ghostview half-hand.g.ps
```

The `-nofold` option draws vertically as much as possible, while the `-noinfo` option removes the signal legend.

3. Generate and display the state graph for your STG using the `write_sg` tool. For that, run the following commands and compare their effects:

```
write_sg half-hand.g | draw_astg -sg | ghostview -
write_sg half-hand.g -o half-hand.sg
draw_astg -nofold half-hand.sg | ghostview -
write_sg -bin half-hand.g -o half-hand.bin.sg
draw_astg -sg half-hand.bin.sg | ghostview -
draw_astg -bin half-hand.bin.sg | ghostview -
draw_astg -sg -noinfo -nonames -bw half-hand.bin.sg | ghostview -
```

The `-bin` option of `write_sg` generates a binary encoding for all states and checks for CSC violations, if any (i.e., pairs of states with the same code and different enabled output signals). The `-bin` option of `draw_astg` understands this notation and highlights violations.

4. Check that the version corresponding to Figure 3 (b) (comment out appropriate lines in the `half-hand.g` file) is unbounded:

```
write_sg half-hand.g -o half-hand.sg
```

5. Check that the version in Figure 3 (c) (un-comment out appropriate lines in the `half-hand.g` file) has CSC-violations:

```
write_sg -bin half-hand.g | draw_astg -bin | ghostview -
```

6. Check that the final version in Figure 3 (d) is directly implementable with a speed-independent circuit:

```
write_sg -bin half-hand.g | draw_astg -bin | ghostview -
```

7. Derive netlists of logic equations for output signals of the final version (Figure 3 (d)) and the third version (Figure 3 (c)) using the `-cg` option of `petrify` (that generates one complex gate per output signal). Examine the equations (`half-hand.cg.eqn`) and the output STG (`half-hand.out`) files. Note where `petrify` introduces an additional signal `csc0` to resolve CSC-conflicts in the third version (Figure 3 (c)).

```
petrify half-hand.g -cg -eqn half-hand.cg.eqn -o half-hand.out
more half-hand.cg.eqn
draw_astg half-hand.out | ghostview -
```

Note also how `petrify` removed the redundant arc  $Ri^+ \rightarrow Ao^+$  in the `half-hand.out` output STG.

The implementation that `petrify` obtained for the STG with increased concurrency and the CSC problem in this case has exactly the same complexity (but a slightly different form) as the one obtained for the case without the CSC problem. This does not happen in general, and concurrency reduction is often a good way to trade off logic complexity and performance.

8. Derive implementations for generalised C-elements<sup>1</sup> using the `-gc` of `petrify` (you can also prevent `petrify` from generating the output STG file by using option `-no` instead of `-o`) and examine the `petrify.log` report file about alternative implementations.

```
petrify half-hand.g -gc -eqn half-hand.gc.eqn -no
more half-hand.cg.eqn
more petrify.log
```

The `petrify.log` file also reports technology-independent performance information such as:

- Average and maximum number of output events between any ordered pair of input events. If input events are considered “slow” then this determines in a very abstract manner (by considering all GC elements to have the same delay) the performance of the system, and is determined only by the input specification. In the part of the file labeled `Input -> Input Delays` the numbers in parentheses denote the number of output events between the corresponding pair of input events. You should look at the output STG to understand the numbers, and consider that the path  $Ri^+ \rightarrow Ro^+ \rightarrow Ao^+ \rightarrow Ro^- \rightarrow Ai^+$  is not a worst-case path under the hypothesis of slow input events, because  $Ai^+$  will always determine the firing time of  $Ro^+$ .

<sup>1</sup>I.e., logic blocks of the form  $y = ab + ay + cy$  where  $a, b$  and  $c$  can be arbitrary product terms. These generalised C-elements have a very efficient transistor-level implementation (cf. lecture notes).

- Estimated delays for individual synthesized gates (when several alternatives exist and have been explored by `petrify` in its search they are all listed), based on the length of transistor stacks. More details about the delay model used in Petrify can be found on the `petrify` manual page (type `man petrify`; scroll till option `-gcmodel`).
9. Derive implementation for the library of three-input gates using `-lit3` option and then for the library of two-input gates using `-lit2` option. Compare the implementation for signal `Ao` (or `csc0`). Try to explain why it is different. For this exercise you will need the library description file `petrify.lib` (also included in the solutions directory) in your current directory.

```
petrify half-hand.g -lit3 -tm -eqn half-hand.lit3.eqn -no
petrify half-hand.g -lit2 -tm -eqn half-hand.lit2.eqn -no
more half-hand.lit3.eqn
more half-hand.lit2.eqn
```

Note that if we only use `-tm` (technology mapping), `petrify` generally decomposes logic until some gate is found that matches each signal (modulo inverters). If `-lit3` `-tm` is used, then we force decomposition into 3-literal functions, and then technology mapping is applied. In general, it is not clear what the best option out of `-litN` is. Sometimes, doing a more aggressive decomposition allows a better sharing of gates. Another reason for improvement is that finer decomposition allows a better exploration for matching gates by trying to collapse with different neighbours. A reason for worse results is that more decomposition may require extra acknowledgement wires.

10. Find implementation using only C-elements as asynchronous latches. Use `-latch C` option.

```
petrify half-hand.g -latch C -tm -eqn half-hand.cel.eqn -no
more half-hand.cel.eqn
```

11. Find implementation without C-elements using `-latch SRD` option (selecting Set- and Reset-dominant S/R latches as well as D latches).

```
petrify half-hand.g -latch SRD -tm -eqn half-hand.srd.eqn -no
more half-hand.srd.eqn
```

Note that in the actual implementation we can use the inverted version of [1] (hence have a three-input NOR instead of OR) and apply it directly to the input of the Set-dominant latch for [Ro]. Note also that the output of the *inverter* gate [0] is not acknowledged (when switching from 0 to 1), and hence its delay must be smaller than that of the rest of the logic (labelled as PRAGMA in file `half-hand.srd.eqn`). In particular, if it is slow in going from 0 to 1, signal [1] (in its inverted implementation) might have a  $0 \rightarrow 1 \rightarrow 0$  hazard as a result of `Ao`-after `Ai`- when it is still [0]=0. This hazard may propagate to the primary output [Ro].

12. Find implementation without latches at all, using combinational gates with possible feedbacks using `-nolatch` option. Observe the result of signal insertion (`map0`) into the STG using `draw.astg` utility.

```
petrify half-hand.g -nolatch -tm -eqn half-hand.nolatch.eqn -o half-hand.out
more half-hand.nolatch.eqn
draw_astg half-hand.out | ghostview -
```

To summarise our use of latches, here is the comment from the `petrify` manual page. The `-latch str` option specifies a restricted set of latches to be used for synthesis; `str` can contain any string of characters from the set CDRS, which respectively correspond to the following latches: Muller C element, D latch, reset-dominant SR latch and set-dominant SR latch. These latches are *only used if found* in the library. In case this option is not specified, any asynchronous latch in the library is used.

13. Find a timed circuit implementation using the relative timing option `-topt`. Specify timing constraints for `half-hand.g` based on the assumption that input events are slower (i.e. occur later) than the output events that have common predecessors (and exactly the same predecessors) with those inputs, e.g. `.time Ao+<|Ai+`, which corresponds to introducing a partial fundamental mode. Examine the contents of report file `petrify.log`. In this case there is only one timing constraint, so `petrify` either uses it or does not. In general, only some constraints might be needed to justify the correctness of a given solution.

```
petrify half-hand.g -topt -cg -eqn half-hand.topt.cg.eqn -no
more half-hand.topt.cg.eqn
more petrify.log
```

Explain why adding other timing assumptions between inputs and outputs, such as `.time Ao-<|Ai-` and `.time Ro-<|Ri-`, may be wrong if we have no more information about relative timing between the left and right hand side parts of the environment.

## 2 Task 2: 2-to-4 and 4-to-2 phase converters

### 2.1 What are 2-to-4 phase and 4-to-2 phase converters?

Figure 4 depicts the interface of 2-to-4 and 4-to-2 phase converters.

A 2-to-4 phase converter can be described by the following regular expression:

$$(req2; req4+; ack4+; req4-; ack4-; ack2)^*$$

Here events `req2` and `ack2` stand for either rising or falling transitions on the 2-phase handshake.

A 4-to-2 phase converter can be described similarly by the following regular expression (as well as by other, more concurrent, specifications described in the 4-to-2 exercise):

$$(req4+; req2; ack2; ack4+; req4-; ack4-)^*$$

 


Figure 4: 2-to-4 and 4-to-2 phase converters

## 2.2 Exercise

### 2.2.1 Part 1: 2-to-4 phase converter

1. Specify the behavior of a 2-to-4 phase converter in astg format. Save this specification in file `conv24.g`. (Alternatively, find a sample solution `conv24.g` in directory `solutions` and examine it carefully.)
2. Check if your STG has CSC-violations:

```
write_sg -bin conv24.g | draw_astg -bin | ghostview -
```

3. Obtain STG specifications with only rising (+) and falling (-) transitions, using the `-untog` option):

```
petrify -untog conv24.g -o conv24.untog.g
draw_astg conv24.untog.g | ghostview -
```

4. Resolve CSC-conflicts manually and compare the solution with the one given by `petrify`. For the latter, use the following script:

```
petrify conv24.g -cg -eqn conv24.cg.eqn -o conv24.out
more conv24.cg.eqn
draw_astg conv24.out | ghostview -
```

5. Obtain an implementation with SRD latches:

```
petrify conv24.g -latch SRD -tm -eqn conv24.srd.eqn -no
more conv24.srd.eqn
```

Note that in this example, `petrify` is overly conservative about zero-delay inverters (cf. `PRAGMA` in front of [2]). The output of [2] is actually acknowledged: we have to re-draw the circuit in `conv24.srd.eqn` in such a way that [2] is connected to both the `OAI12` gate for `[req4]` but also to the `NAND2` gate for [1] (instead of `req2` being listed there. Indeed, `[1] = [2]' + csc0'` would have been a much 'cleaner' `NAND2`. With a bit more thought, one can recognise that the combination of `NAND2` [1] and `OAI12` `[req4]` implements an `XOR2` function.

6. Derive monotonic covers for the output signals (`petrify -mc`):

```
petrify conv24.g -mc -eqn conv24.mc.eqn -no
more conv24.mc.eqn
```

Compare this solution with the previous one.

### 2.2.2 Part 2: 4-to-2 phase converter

Figure 5 shows three different specifications for a 4-to-2 phase converter, with different degrees of concurrency between inputs and outputs. The third version has the highest potential performance, because it has only one output transition between any two input transitions, and it performs the 4-phase reset (`ack4+` and `req4-`) completely in parallel with the 2-phase handshake. Of course, its logic cost is also greater.

 


Figure 5: Specifications of 4-to-2 phase converters.

1. Obtain an STG specification for each one of them (the example shows that for Figure 5.(a)) with only rising (+) and falling (-) transitions (use the `-untog` option in `petrify`):

```
petrify -untog conv42_seq.g -o conv42_seq.untog.g
draw_astg conv42_seq.untog.g | ghostview -
```

2. Derive a netlist for each one of the specifications (the example shows that for Figure 5.(c)) using:

```
petrify conv42_par.untog.g -cg -eqn conv42_par.eqn -o conv42_par.out
more conv42_par.eqn
draw_astg conv42_par.out | ghostview -
```

Note how the number of CSC conflicts, and hence the number of state signals and the logic complexity, grows with the increase in concurrency. As usual, performance increase roughly implies area increase.

- Derive a netlist for the same specification (the example shows that for Figure 5.(c)) using timing assumptions, such as simultaneity conditions:

```
.time req2-=ack4+/1@ack2-,req4-/1
.time req2+=ack4+@ack2+,req4-
```

The first constraint means that for both `ack2-` and `req4-/1` the firing times of `req2-` and that of `ack4+` are undistinguishable. Hence `ack2-` could be enabled by `req4-/1` just as well (instead of `req2-` as in the original specification) *without changing the observable firing sequences*.

For that, use:

```
petrify conv42_par.untog.g -topt -cg -eqn conv42_par.t.eqn -o conv42_par.t.o
more conv42_par.t.eqn
draw_astg conv42_par.t.o | ghostview -
```

Compare the solutions with the untimed implementation.

Examine the contents of the `petrify.log` report file.

### 3 Task 3 (advanced): VME bus controller

Figure 6 depicts the interface of a slave device to a VME bus. What is shown here is the result of an abstraction of the main synchronization core between the bus and the device links, separately from all remaining logic. The latter performs address and opcode decoding, error detection and some other functions that are outside this controller.

The behavior of the controller is as follows: a request to read from or write into the device is received by one of the signals `DSr` or `DSw` respectively. In a read cycle, a request to read is sent to the device through signal `LDS`. When the device has the data ready (`LDTACK`), the controller must open the transceiver to transfer data to the bus (signal `D`, which is a Data Enable signal; it controls the transceiver together with a direction signal provided in the bus, namely it closes one latch and opens the tri-state in one direction, and opens the other latch in the other). In the write cycle, data is first transferred to the device by opening the transceiver (`D`). Next, a request to write is sent to the device (`LDS`). Once the device acknowledges the reception of the data (`LDTACK`) the transceiver must be closed to isolate the device from the bus. Each transaction must be completed by a return-to-zero of all interface signals, seeking for a maximum parallelism between the bus and the device operations.

- Construct an STG specifying the behavior of the VME bus controller.
- Solve CSC using `petrify`.
- Obtain a complex gate implementation of the circuit (option `-cg`).

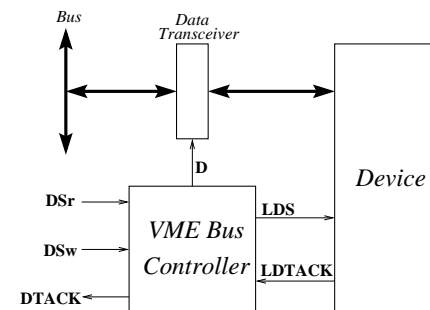


Figure 6: VME bus controller

- Derive a netlist of gates by first decomposing the circuit into 3-input gates and the mapping onto a gate library (`-lit3 -tm`).
- Optimize the implementation (option `-topt`) by adding relative timing constraints to your STG model, such as the assumption that the bus and device handshakes are slow compared to output and internal signal transitions.
- Modify** the specification of the VME bus controller in such a way that, instead of two ‘dual-rail’ input strobes `DSw` and `DSr` (an “already decoded” version), the interface to the bus consists of a single strobe `DS` and an opcode signal (`WR`). The value of `WR` determines what operation the controller is suppose to start when strobe `DS` goes high. Let it be write if `WR = 1` and read if `WR = 0`. We can assume about the environment that when the `DS` is low the value of `WR` can arbitrarily change but as soon as the `DS` goes high the state of the `WR` is stable. (**Hint.** Use a pair of complementary places to represent the state of `WR`. The token between these places can toggle by transitions `WR+` and `WR-` only when the value of `DS` is zero. Thus the firing of transition `DS+` must disable transitions `WR+` and `WR-`. This disabling does not lead to output-nonpersistence because both `WR` and `DS` are inputs.)
- Obtain a complex gate implementation for the modified STG. Compare it with the previous solution.