

# **Asynchronous Computing**

## **(Electronic Designer's perspective)**

Alex Yakovlev  
Newcastle University  
Newcastle upon Tyne, U.K.

<http://async.org.uk>

<http://workcraft.org>


# Outline

- Simple intro examples on whiteboard
- Six Asynchronous Design Principles:
  - Asynchronous Handshaking
  - Delay-insensitive Encoding
  - Completion Detection
  - Causal Acknowledgement
  - Full Indication and Early Evaluation
  - Time Comparison
- Pros and Cons
- (Some of the) Models, Techniques and Tools for Asynchronous Design
- Asynchronous Design from Signal Transition Graphs

# Asynchronous Behaviour

- **Synchronous vs Asynchronous behaviour in general terms, examples:**
  - Orchestra playing with vs without a conductor
  - Party of people having a set menu vs a la carte
- **Synchronous means all parts of the system acting globally in tact, even if some or all part 'do nothing'**
- **Asynchronous means parts of the system act on demand rather than on global clock tick**
- **Acting in computation and communication is, generally, changing the system state**
- **Synchrony and Asynchrony can be in found in CPUs, Memory, Communications, SoCs, NoCs etc.**

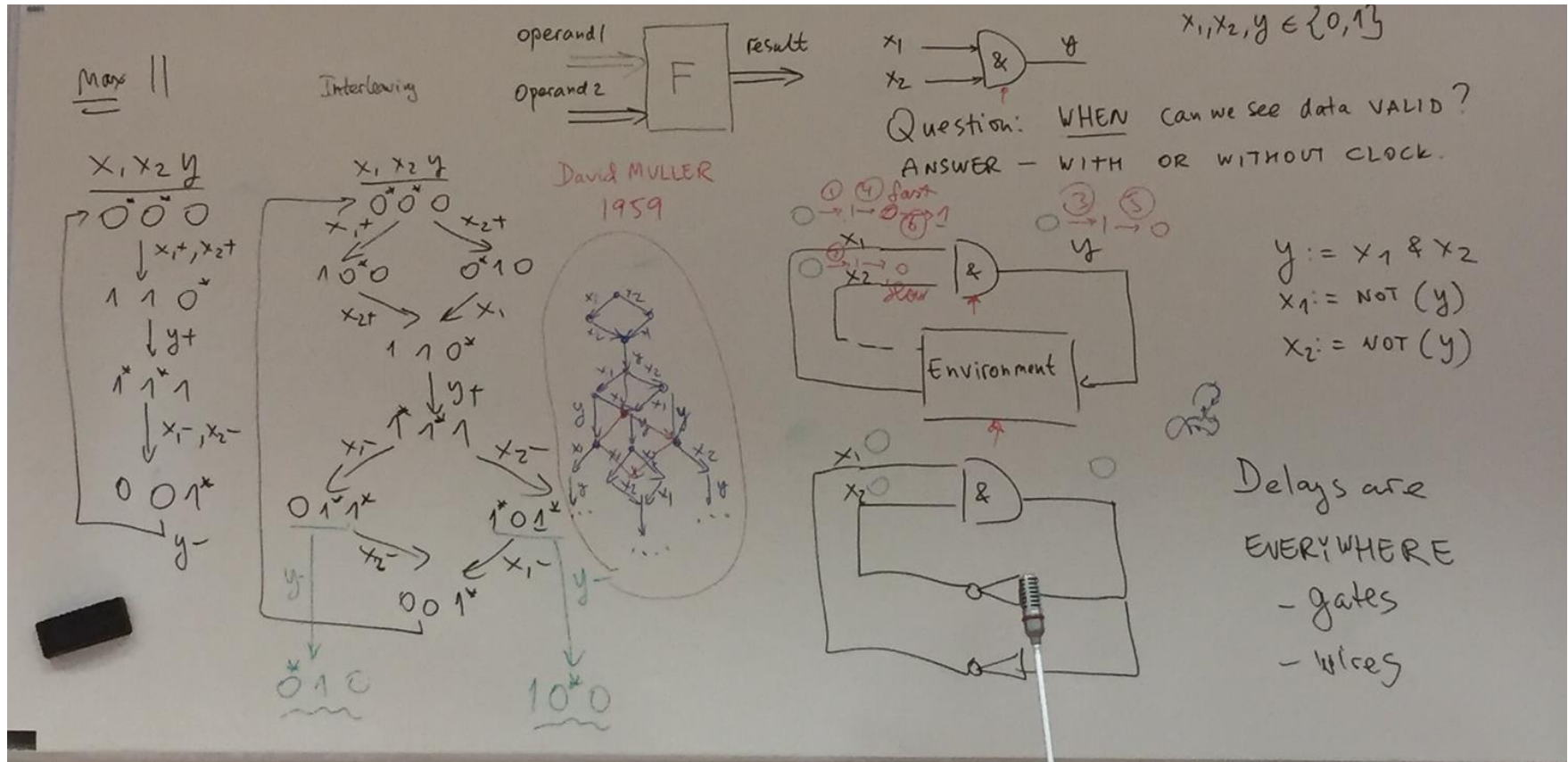
# Introduction/Motivation: Simple example



# Key Principles of Asynchronous Design

- **Asynchronous handshaking**
- **Delay-insensitive encoding**
- **Completion detection**
- **Causal acknowledgment (indicatability)**
- **Strong and weak causality (full indication and early evaluation)**
- **“Time comparison” (synchronisation, arbitration)**


# Why and what is handshaking?

 

**Mutual Synchronisation is via Handshake**


# Synchronous clocking

**How we think**

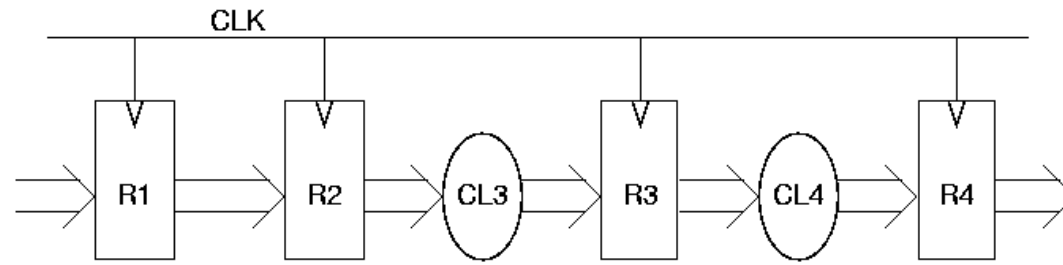

(a)


**What we design**

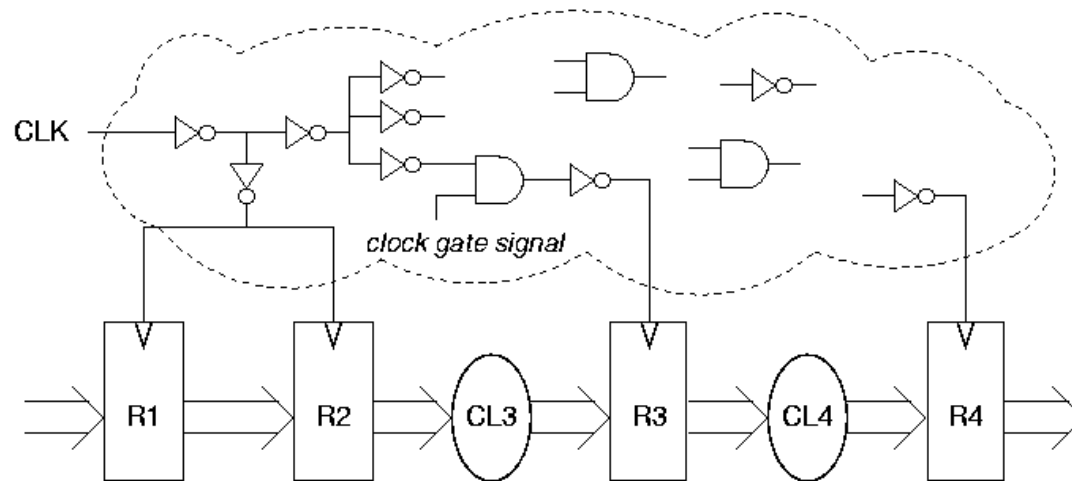


(b)

# Asynchronous handshaking

# What we design

 


# How we think

 




# Handshake Signalling Protocols


## Level Signalling (RTZ or 4-phase)

 


(a)

 
 
## Transition Signalling (NRZ or 2-phase)



 
# Why and what is delay-insensitive coding?




**Data Token = (Data Value, Validity Flag)**


# Bundled Data

 


Return to Zero:

 

**Non-Return-to-Zero**

 


# Delay-Insensitive encoding (Dual-Rail)

 


NRZ coding leads to complex logic implementation; special ways to track odd and even phases and logic values are usually needed

**RTZ:**

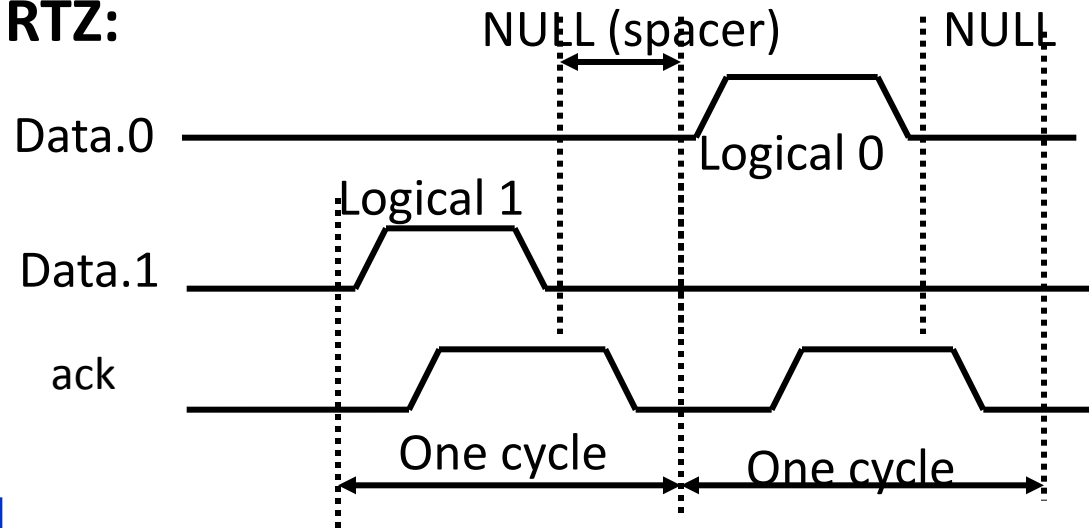


**NRZ:**

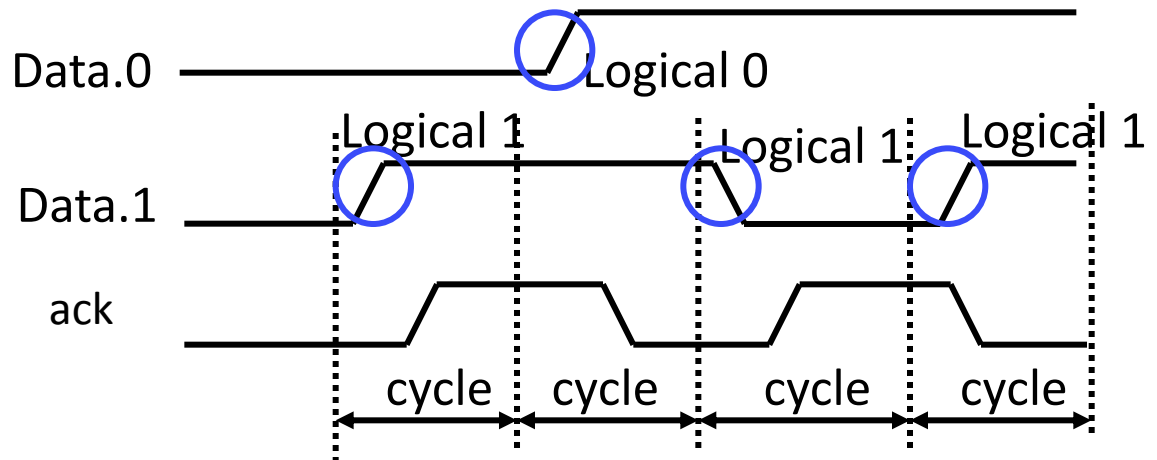

# DI codes (1-of-n and m-of-n)


- **1-of-4:**
  - 0001=> 00, 0010=>01, 0100=>10, 1000=>11
- **2-of-4:**
  - 1100, 1010, 1001, 0110, 0101, 0011 – total 6 combinations (cf. 2-bit dual-rail – 4 comb.)
- **3-of-6:**
  - 111000, 110100, ..., 000111 – total 20 combinations (can encode 4 bits + 4 control tokens)
- **2-of-7:**
  - 1100000, 1010000, ..., 0000011 – total 21 combinations (4 bits + 5 control tokens)

# Why and what is completion detection?

 

**Signalling that the Transients are over**

# Bundled-data logic blocks

 


Completion  
is implicit:  
by done  
signal

The delay must  
scale with the worst  
case delay path,  
So ... not really self-  
timed


**Conventional logic + matched delay**

# True completion detection

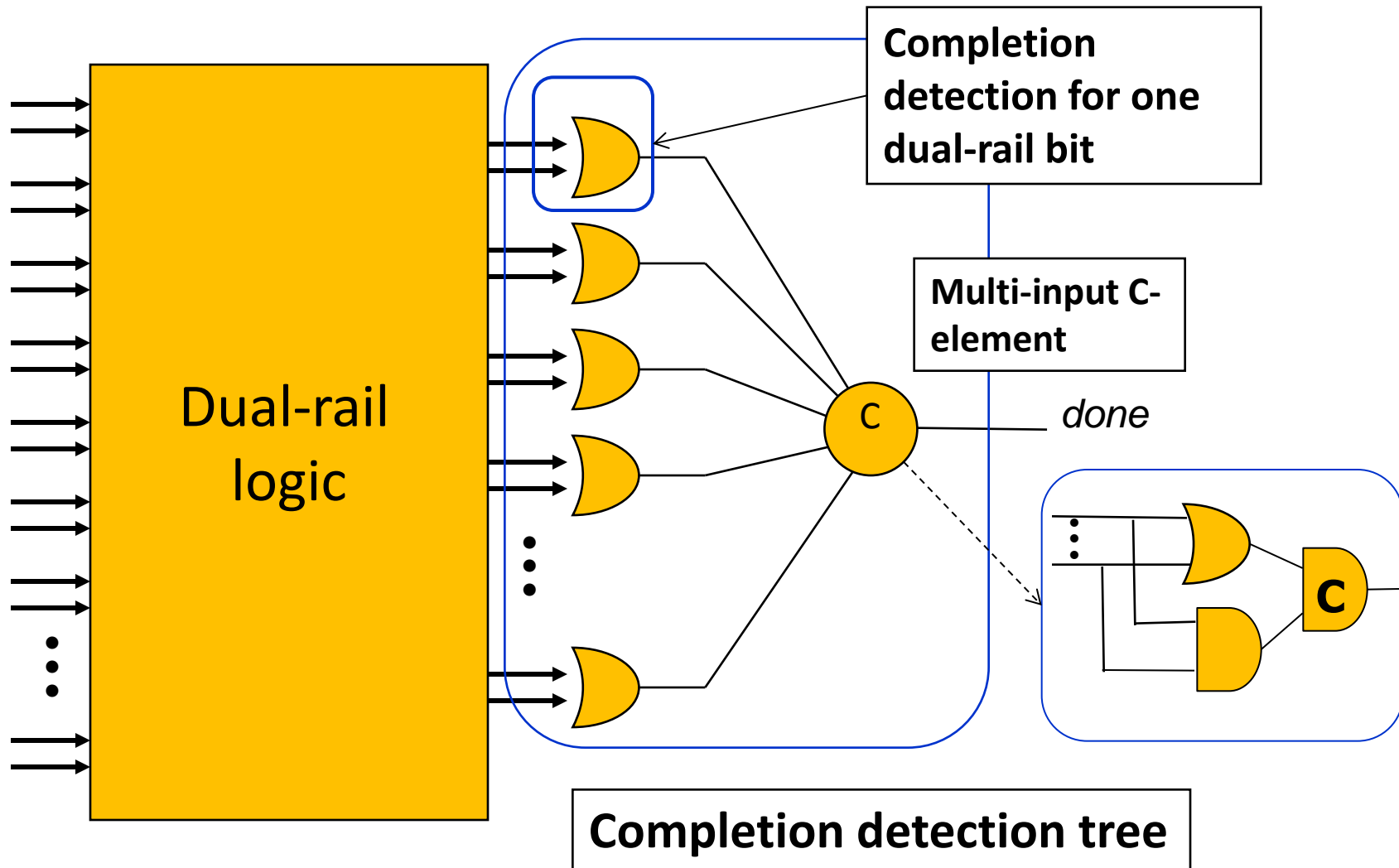




# The Muller C element

 

$$Z_{\text{next}} = AB + Z(A + B)$$

A	B	Z <sup>+</sup>
0	0	0
0	1	Z
1	0	Z
1	1	1


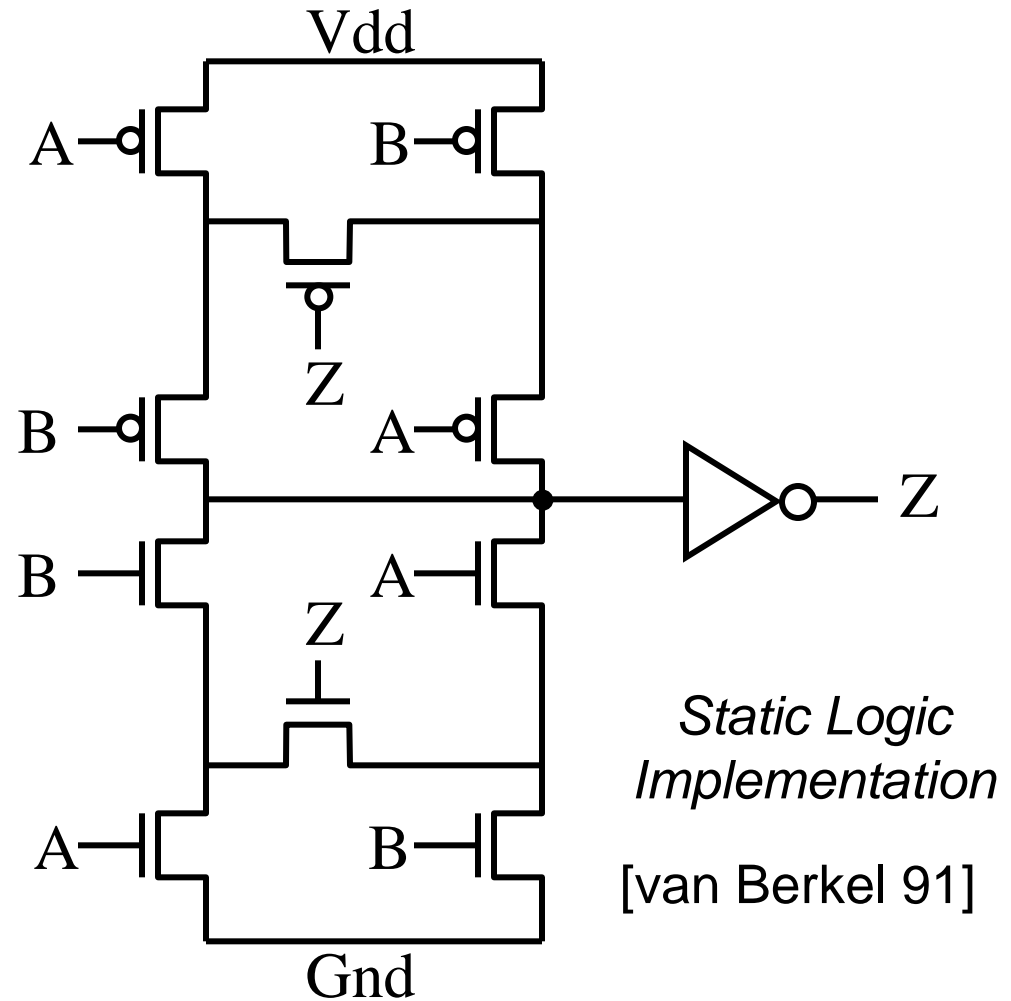


# Why and what is causal acknowledgment?




**Every signal event must be acknowledged by another event**

# Causal acknowledgment

 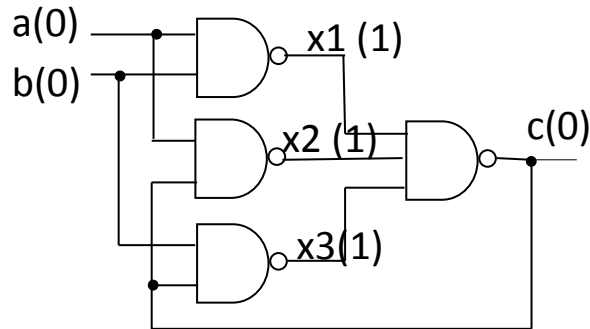


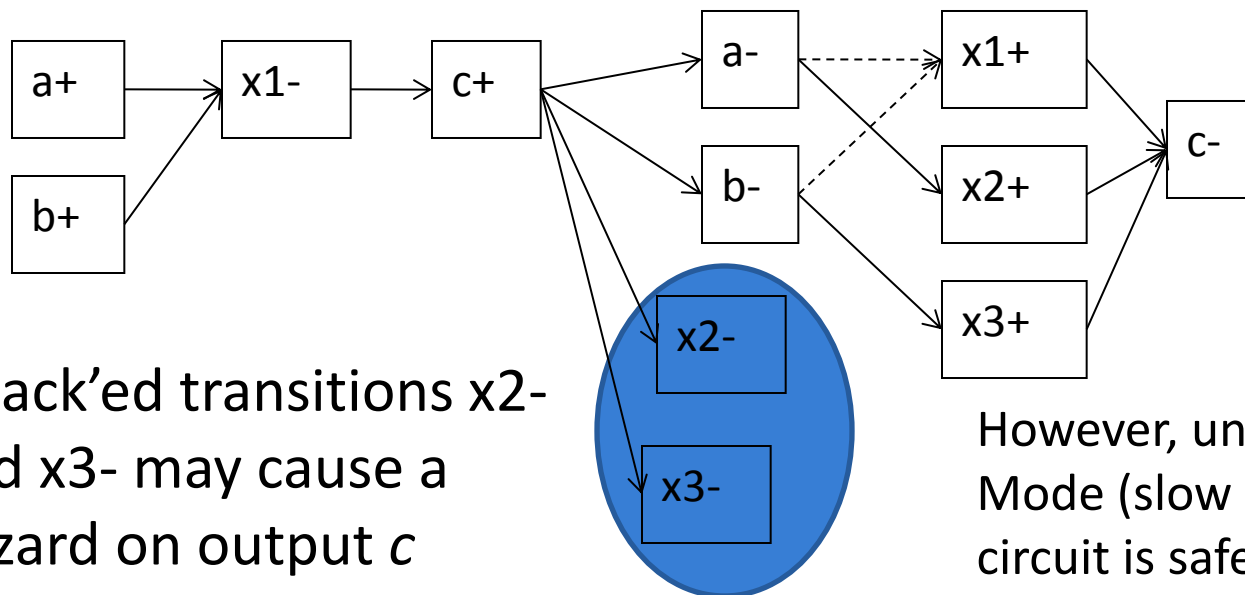
C-element implementation using simple gates





Unack'ed transitions  $x2-$  and  $x3-$  may cause a hazard on output  $c$

However, under Fundamental Mode (slow environment) the circuit is safe

# Principle of causal acknowledgement

  


  C-element implementation using simple gates



Each transition is causally ack'ed, hence no hazards can appear

 
# Why and what are strong and weak causality ?




**Degree of necessity of precedence of some events for other events**
 
# Strong Causality

- Petri net transitions synchronising as rendez-vous



 
- Logic circuits: Muller C-element (in 0-1 and 1-0 transitions), AND gate (in 0-1 transitions), OR gate (in 1-0 transitions)




A	B	C <sup>+</sup>
0	0	0
0	1	C
1	0	C
1	1	1
 
# Weak Causality


- Petri net transitions communicating via places



 
- Logic circuits: AND gate (in 1-0 transitions), OR gate (in 0-1 transitions)


 
# Full indication versus Early Evaluation



 Dual-rail AND gate  
with full input  
acknowledgement



Dual-rail AND gate  
with "early propagation"

**Allows outputs to be produced from NULL to Codeword only when some (required) inputs have transitioned from NULL to Codeword (similar for Codeword to NULL)**



# Why and what is timing comparison?




**Telling if some event happened before  
another event**

# Synchronizers and arbiters

- Synchronizer

Decides which clock cycle to use for the input data


Input

 

- Asynchronous arbiter


Decides the order of inputs

Input 1

 


Input 2

# Metastability is....

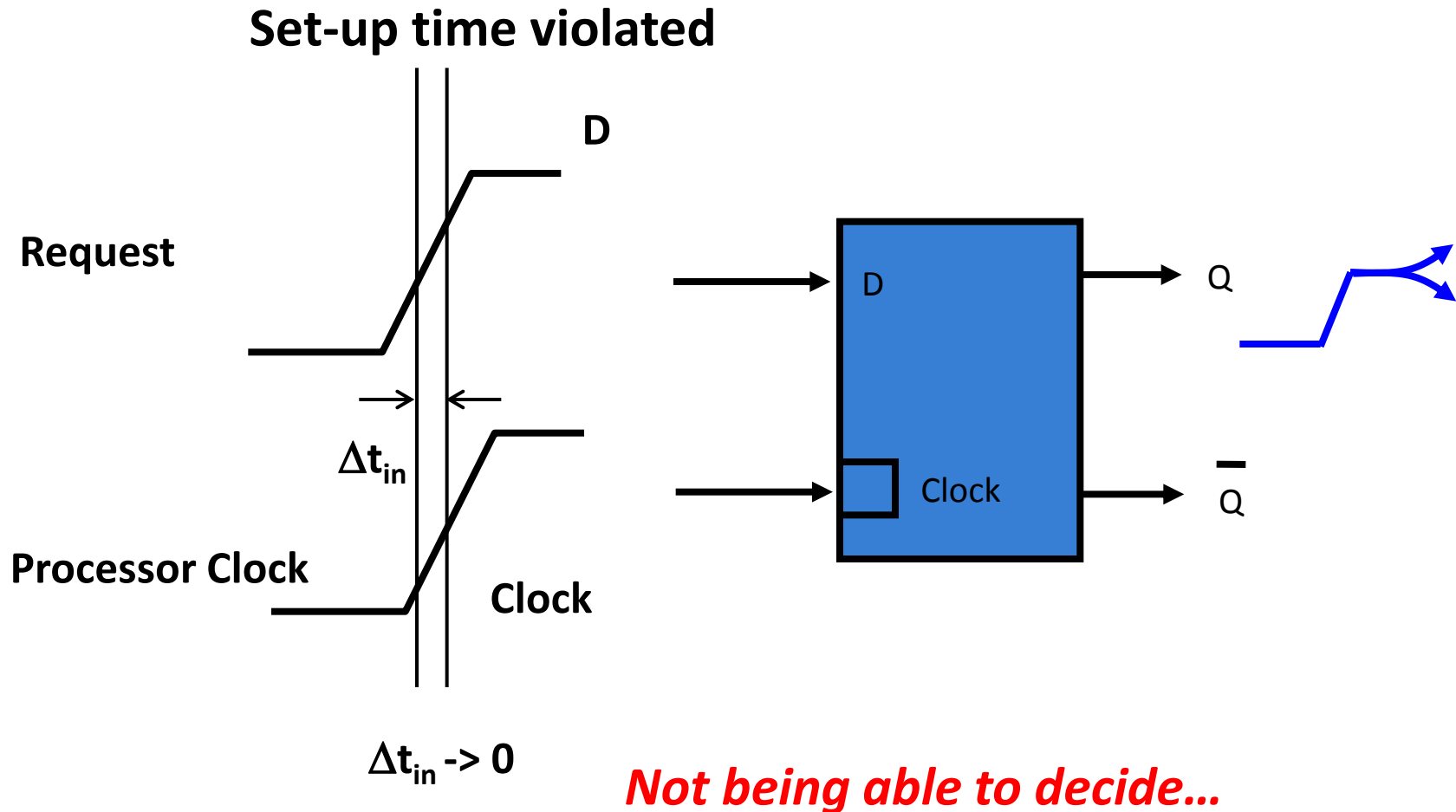


# Typical responses

 

- We assume all starting points are equally probable
- Most are a long way from the “balance point”
- A few are very close and take a long time to resolve
 
# Two-way arbiter (Mutual exclusion element)

Basic arbitration element: Mutex (due to Seitz, 1979)



**An asynchronous data latch with metastability resolver can be built similarly**



# Pros...

- People have always been excited by asynchronous design, and motivated by:
  - **Higher performance** (work on average not worst case delays)
  - **Lower power consumption** (automatic fine-grain “clock” gating; automatic instantaneous stand-by at arbitrary granularity in time and function; distributed localized control; more architectural options/freedom; more freedom to scale the supply voltage)
  - **Modularity** (Timing is at interfaces)
  - **Lower EMI and smoother Idd** (the local “clocks” tend to tick at random points in time)
  - **Low sensitivity to PVT variations** (timing based on matched delays or even *delay insensitive*)
  - **Secure chips** (white noise current spectrum)
  - **Plus, ... a lot of scope and fun for research (there are many unexplored paths in this forest!)**

# ... Cons

- So why have async designers been often “crucified” in the past?
  - **Overhead** (area, speed, power)
    - Control and handshaking
    - Dual-rail and completion detection costs
  - **Hard to design**
    - yes and no, ... It’s different – **there are very many styles and variants to go and one can easily get confused which is better**
  - **Very few \*\*practical\*\* CAD tools** (but many academic tools)
    - Tools are quite specific to particular design styles and design niches; hence don’ t cover the whole spectrum
    - Complexity of timing and performance models
    - Difficulty with sign-off (for particular frequency requirements)
    - ... But the situation is improving
  - **Hard to Test**
    - Possible, but not as mature as sync

# Models and techniques for design

  




# Models and techniques for asynchronous design


- **Models:**
  - Delay model (inertial, pure, gate delay, wire delay, bounded and unbounded delays)
  - Models of environment (fundamental mode, input-output)
  - Models of switching behaviour (state-based, event-based, hybrid)
- **RTL level:**
  - Data and control paths separate (data flow graphs, FSMs, Signal Transition Graphs, Synchronised Transitions)
  - Pipeline based (Combinational logic plus registers and latch controllers, e.g. micropipelines, gate-level pipelining)
  - Process-based (CSP-like, Balsa, Haste, Communicating Hardware Processes)
- **High-level models**
  - Flow graphs (Marked graphs, extended MGs), Petri nets, Markov Chains
  - Behavioural HDLs (C, SystemC)
 
# Gate vs wire delay models

- Gate delay model: delays in gates, no delays in wires




 - Wire delay model: delays in gates and wires


 
# Delay models for async. circuits

- **Bounded delays (BD)**: realistic for gates and wires.
  - Technology mapping is easy, verification is difficult
- **Speed independent (SI)**: Unbounded (pessimistic) delays for gates and “negligible” (optimistic) delays for wires.
  - Technology mapping is more difficult, verification is easy
- **Delay insensitive (DI)**: Unbounded (pessimistic) delays for gates and wires.
  - DI class (built out of basic gates) is almost empty
- **Quasi-delay insensitive (QDI)**: Delay insensitive except for critical wire forks (*isochronic forks*).
  - In practice it is the same as speed independent




# Control Logic


- **Control specification based on Petri nets (Signal Transition graphs)**

# Control specification



Signal Transition Graph  
(STG)

 



Timing Diagram

 



# Control specification

  

# Control specification

 
 


# Control specification

 
 




# Control specification

 
 


# VME bus example using Petri nets

 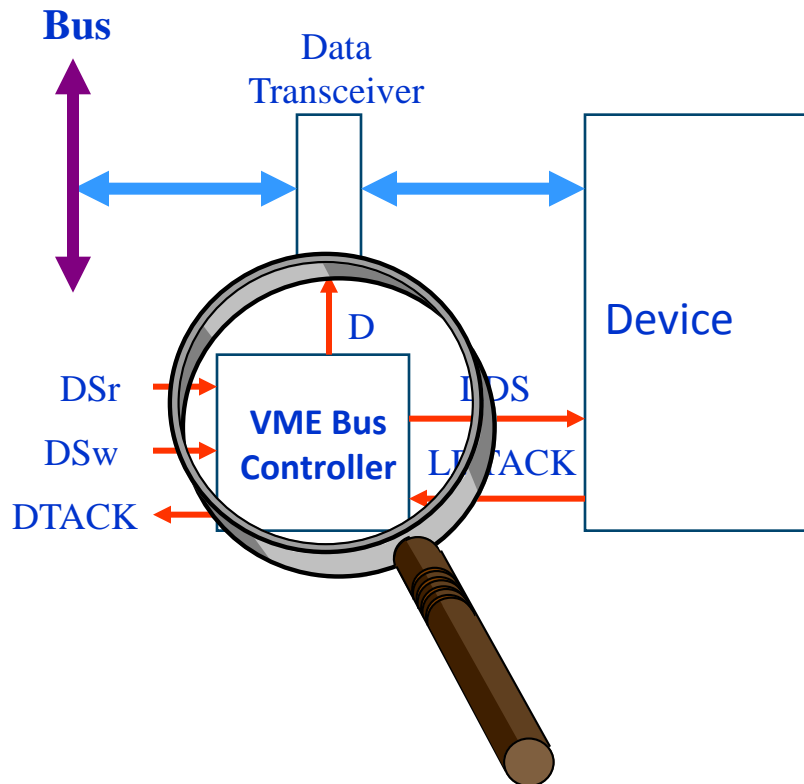


**Read Cycle**


# STG for the READ cycle

 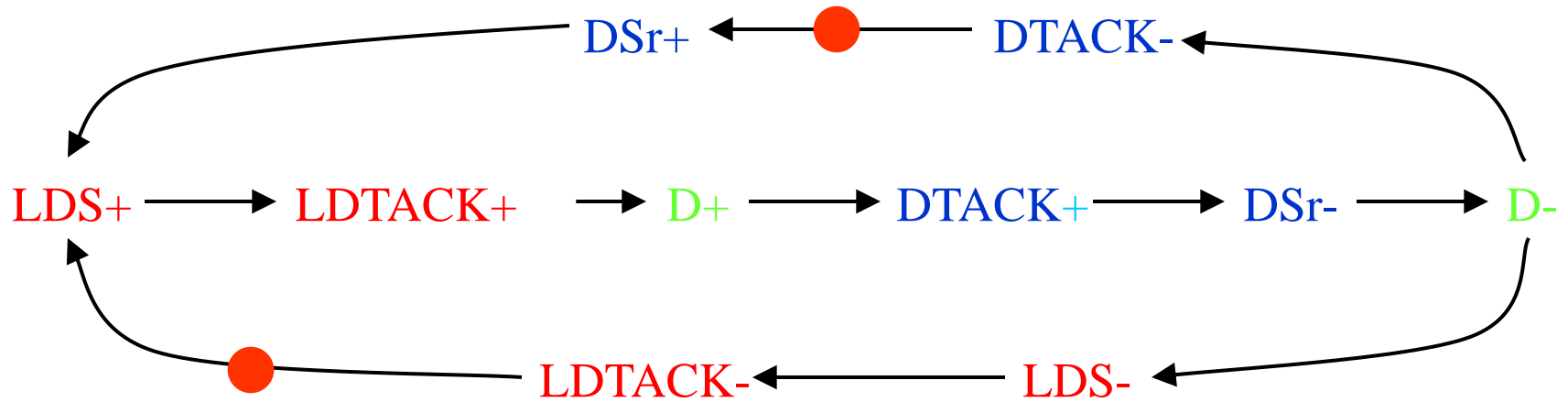

# Choice: Read and Write cycles

 

# Choice: Read and Write cycles

 

# Workcraft tool: [workcraft.org](http://workcraft.org)

- **Framework for interpreted graph models**
  - **Circuits, STGs, state graphs, dataflow structures, ...**
  - **Interoperability between different abstraction levels**
  - **Consistency for users; convenience for developers**
- **Elaborate graphical user interface**
  - **Visual editing, analysis, and simulation**
  - **Easy access to common operations**
  - **Possibility to script specialised actions**
- **Interface to back-end tools for synthesis and verification**
  - **Reuse of established theory and tools (PETRIFY , MPSAT , PUNF )**

# Synthesis & verification of async circuits

Workcraft

File Edit View Utility Help Tools

dfs-all\_elements - Dataflow Structure

control layer

complex ST path

vme\_stg - Signal Transition

DTACK-

DSr+ LDS+ D+ LDS+ DTACK+ D- DTACK+ DSw-

LDs+ LDs- DTACK- LDs+ DTACK+ DSw-

ck on the highlighted transition

mayevsky\_c\_el2 - Digital Circuit

c1 c2 c3 c4

Property editor

N/A

Tool controls

Trace Branch

Trace	Branch
D-/1	
DTACK+/1	
DSw-	
DTACK-	
DSr+	DSw+
LDS-	D+/1
LDs-	LDS-
LDs+	LDs+
LDs+	LDs+/1
D+	LDs+/1
DTACK+	D-/1

Signal State

Signal	State
D	0
DTACK	0
DSw	1
DSr	?
LDS	1
LDs	1

Editor tools

Workspace

Workspace

- External
  - cpog1.work
  - dfs-all\_elements.work
  - mayevsky\_c\_el2.work \*
  - policy-test2.work
  - vme\_stg.work \*
  - xmas-test1.work




Output

```

INORDER = DSr DSw LDs+ DTACK D DTACK LDS csc0;
OUTORDER = [D] [DTACK] [LDS] [csc0];
[D] = DSr LDs+ csc0' + DSw (csc0 + LDs+);
[DTACK] = D' csc0' (DSr' + DSw) + DSw' D;
[LDS] = csc0';
[csc0] = DSr' D' (csc0 + DSw) + LDs+ csc0;

# Set/reset pins: reset(csc0)
moved from Untitled to !External/xmas-test1.work
correcting open file path...
    
```



# Logic synthesis: xyz-example

   



***Signal Transition Graph (STG)***



# Token flow

  

# State graph

  


# Next-state functions

$$x = \bar{z} \cdot (x + \bar{y})$$

$$y = z + x$$

$$z = x + \bar{y} \cdot z$$

 

# Deriving next state functions

## 1) Truth Table

Previous state	Next State
0*0 0	1 0 0
1 0*0*	1 1 1
0 1*0	0 0 0
1 1 0*	1 1 1
0 0*1	0 1 1
1*0*1	0 1 1
0 1 1*	0 1 0
1*1 1	0 1 1

## 2) Boolean Minimization

xy	00	10	11	01
z				
0	1	1	1	0
1	0	0	0	0

$$x = \bar{z} \cdot (x + \bar{y})$$

Observations in this example:

**1) All combinations are used as states**

**2) All states appear uniquely**


**Generally, this is not always the case!**

# Complex Gate netlist

$$x = \bar{z} \cdot (x + \bar{y})$$

$$y = z + x$$

$$z = x + \bar{y} \cdot z$$

 

# Circuit synthesis

- **Goal:**
  - **Derive a hazard-free circuit under a given delay model and mode of operation**

# Speed independence

- **Delay model**
  - Unbounded gate / environment delays
  - Certain wire delays shorter than certain paths in the circuit
- **Conditions for implementability:**
  - Consistency
  - Complete State Coding
  - Persistency

# Implementability conditions

- **Consistency**
  - Rising and falling transitions of each signal alternate in any trace
- **Complete state coding (CSC)**
  - Next-state functions correctly defined
- **Persistency**
  - No event can be disabled by another event (unless they are both inputs)



# Implementability conditions




- **Consistency + CSC + persistency**



- **There exists a speed-independent circuit that implements the behavior of the STG**

**(under the assumption that any Boolean function can be implemented with one complex gate)**

# Persistence

   

59

Speed independence  $\Rightarrow$  glitch-free output behavior under any delay

# Conclusion

- **Asynchronous design is based on rigorous principles of causality and concurrency**
- **It allows electronic circuits to operate without centralised time constraints and adapt to any structural or behavioural variations and noise**
- **Nature is largely asynchronous as it is typically structured around energy supplies; synchronisation takes place in a distributed way**
- **Research question: Are reaction systems asynchronous? And in what way they are or can be asynchronous?**
- **Attend the workshop on “Bringing Asynchrony to Reaction Systems”!**
- **I encourage development of a Reaction Systems modelling plug-in under Workcraft.org**