

LSS1 Examples Sheet 1

1. Figure 1 shows a circuit using an operational amplifier. Determine I and V_o .

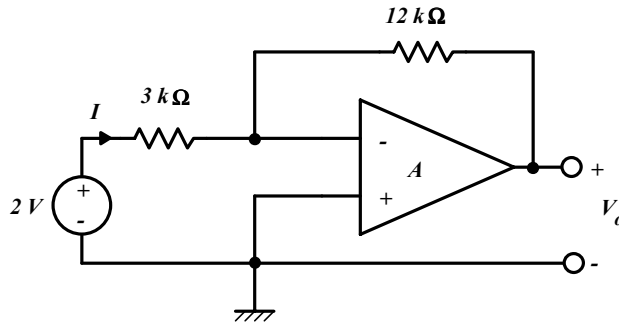


Figure 1

2. Using an ideal operational amplifier and two resistors only, design an inverting amplifier circuit with a gain of 6 and input impedance of $15\text{ k}\Omega$.
3. Figure 2 shows a circuit using an ideal operational amplifier. If it is required that $V_o = 2V_1 + 5V_2$, determine suitable values for R_1 , R_2 and R_3 .

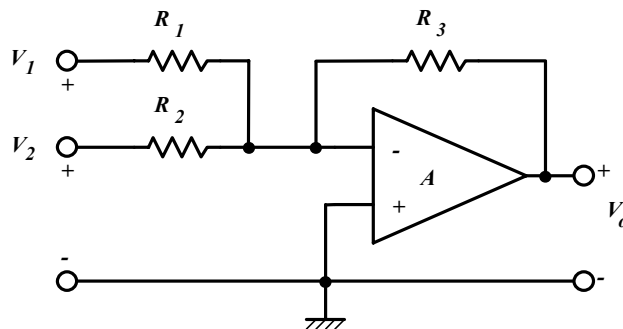


Figure 2

4. For the circuit and input signal shown in figure 1, sketch the shape of the output waveform.

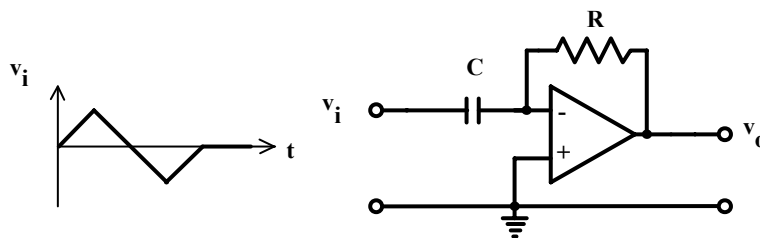


Figure 3

5. For the integrator circuit, determine suitable values for R and C if $\tau = 1\text{ ms}$.
6. An amplifier has the following frequency response function:

$$G(\omega) = \frac{10}{1 + j\omega/200}$$

Calculate the gain and phase shift of this circuit at a frequency of 100 rad/s .